22419

21819 3 Hours / 70 Marks

Seat No.

Instructions –

- (1) All Questions are Compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary.
- (5) Use of Non-programmable Electronic Pocket Calculator is permissible.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIV<u>E of t</u>he following:

10

- a) List standard voltage level used in India.
- b) Define: voltage regulation of transmission line.
- c) State the disadvantages of skin effect.
- d) State four HVDC transmission line route on India with their voltage level.
- e) Define: primary and secondary distribution system
- f) State the classification of distribution substation.
- g) State any four properties of conductor material used for overhead conductor.

22419 [2]

		Marks
2.	Attempt any TH <u>REE of t</u> he following:	12
	a) Explain any four advantages of high voltage power transmission.	
	b) Describe the proximity effect and state its two disadvantages.	
	c) Draw and explain Bi-polar HVDC transmission line.	
	d) State the different methods of improving string efficiency. Explain any one method in detail.	
3.	Attempt any TH <u>REE of t</u> he following:	12
	a) Draw the single line diagram of AC electric transmission and distribution system.	
	b) Explain the Ferrantio effect in detail.	
	c) Explain the grid system of distribution and state its advantages.	
	d) Draw and explain the construction of underground cables.	
4.	Attempt any TH <u>REE of t</u> he following:	12
	a) State the classification of transmission lines based on voltage level and length of lines.	
	 b) Draw the circuit diagram and phasor diagram of nominal T method of medium transmission line. 	
	c) State the limitations of EHVAC transmission line.	
	d) Draw the single line diagram (layout) of 33/11 kV substation.	
	e) Explain the shackle type insulator with neat sketch.	

22419 [3]

12

12

- 5. Attempt any TWO of the following:
 - a) Discuss the effect of transmission line parameters on the performance of transmission line (any six points).
 - b) Explain the features of flexible AC transmission line (any four). State types of FACTS controller.
 - c) A single phase AC distributor AB 300 M long is fed from end A and is loaded as under.
 - (i) 100 A at 0.707 pf lagging 200 m from point A.
 - (ii) 200 A at 0.8 pf lagging 300 m from point A The load resistance and reactance of the distributor is 0.2Ω and 0.1Ω per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.
- 6. Attempt any TWO of the following:
 - a) A 3 phase line of 4 km length delivers 4000 kW at a p.f of 0.8 lagging to a load the resistance and reactance per km of each conductor are 0.2 Ω and 0.5 ohm respectively if the voltage at the supply end is maintained at 11 kV. Calculate the received end voltage and efficiency of line.
 - b) Each line of a 3 ph system is suspended by a string of 3 similar insulators. If the voltage across the line unit is 17.5 kV, calculate the line to neutral voltage. Assume that the shunt capacitance between each insulator and earth is 1/8th of the capacitance of insulator itself. Also find the string efficiency.
 - c) Draw the symbols and state their function of components used in substation (any six).

SUMMER-2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 1 of 28

Important suggestions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance. (Not applicable for subject English and communication skills)
- 4) While assessing figures, examiner may give credit for principle components indicated in a figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case some questions credit may be given by judgment on part of examiner of relevant answer based on candidate understands.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q.1	Attempt any FIVE of the following 10 Marks
a) Ans: :	List standard voltage level used in India. Standard voltage level used in India: (2 Marks)
	☐ Generation Voltage: 3.3KV, 6.6KV,11KV and 17.5 KV,21KV (Now a days generation voltage is in the range of 11KV- 33KV)
	☐ Primary Transmission voltage :- 220 KV, 400KV, 765 KV (750 KV)
	☐ Secondary Transmission voltage :- 220 KV, 132 KV, 110 KV, 66 KV
	 Primary Distribution voltage: 33 KV, 22KV, 11 KV and for long distance line it may be 66 KV
	☐ Secondary Distribution voltage: - 3-phase, 400 Volt, for single phase 230 Volt.
	OR
	□ Standard Transmission voltages in India are 765 KV (750KV), 400KV, 220KV, 132KV, 110KV, 66KV, 33KV, 22KV, 11KV.
b)	Define: voltage regulation of transmission line.
Ans:	voltage regulation of transmission line: (2 Marks)
ı	Voltage regulation is nothing but voltage drop in transmission line expressed in

SUMMER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 2 of 28

	.,				OGO: 7 IIIOWO	4			_ 0 0
	% of rec	eiving e	nd volta	ge					
	%	Regula	ition = -	Sending	End Voltage [Receiving	Recei	ving End Voltage ltage	□100	
	%re	gulat	tion =	$\frac{No\ lo}{}$	ad recei	ving -	end voltage	-	Full loa
c)	State the d	lisadvai	ntages o	f skin effe	ect.				
Ans:						expect	ed: 1 Mark each	. Total	2 Marks)
,	1. Full	cross se	ection of	conducto	r is not utiliz	ed, The	erefore effective		
	redu	ices so	its resis	stance inc	creases (Sin	iceRЩ A)		
	2. Due t	o increa	ase in res	sistance, c	copper losse	s incre	ases (Since copp	er loss	es = I 2R)
	3. So tra	3. So transmission efficiency reduces.							
	4. Due t	4. Due to increase in resistance, Voltage drop increases (Since Voltage drop = I R)							
	5. So vo	ltage re	egulation	becomes	poor (increa	ases)			
۹/ (State four U	VDC tr	nemicci	on line re	vuta an India	- with	thair valtaga lav	ما	
							their voltage leve	eı.	
Ans:	HVDC train	211112210	ni iiile i c		ndia with the		age level. ted: 1/2 Mark ea	ch To	tal 2 Marke)
				(Ally	roui point	expec	teu. 172 iviai k ea	CH, TO	tai Z iviai KS)
		S.N.	From				То		
		1	Rihand	Talcher	Chandrapui	 r	Dadri		
		2	Bersoo		Connecting		Kolar		
				, ,		•			
		3	1	n region m- Pusav	(ilev		Padghe		
		4	(SaSafa	III- FUSAV	vali)		Lower Sileru		
		5					Eastern Region		

SUMMER-2019 Examinations

Su	bject Code: 2	2419	<u>Model Answer</u>	ŀ	Page 3 of 28
		6	Connecting Northern region (Vindhyachal)	Western Region	
		7	Connecting Southern region (Chandrapur)	Western Region	
		8	Connecting Southern region(Vizag- Gajuwaka)	Eastern Region	
e)	Define: prim	ary an	d secondary distribution system		
Ans:	i) Primary I	Distrib	ution:		(1 Mark)
	It is a	3-phas	se, 3-wire transmission line connecte	ed in between receivi	ing substation to

Distribution substation. OR It is link between receiving substation & distribution transformer

ii) Secondary Distribution:

(1 Mark)

It is a 3-phase, 4-wire Distribution line in between Distribution substation to consumer line. OR It is link between distribution transformer substation & consumer.

State the classification of distribution substation.

The classification of distribution substation. Ans:

(Any Four point expected: 1/2 Mark each, Total 2 Marks)

- 1 Pole mounted distribution substation
- Plinth mounted distribution substation
- 2 Compact/prefabricated distribution substation
- Underground distribution substation
- Indoor distribution substation 3 Outdoor distribution substation
- Mobile distribution substation 4

5

SUMMER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 4 of 28

	state any four properties of conductor material used for overhead conductor.
Ans:	Following are the properties of conductor material:-
	(Any Four point expected: 1/2 Mark each, Total 2 Marks)
	1. High conductivity:- Material should have high conductivity
	2. High mechanical strength:- Material should have sufficiently high mechanical
	strength
	3. Flexible :- Material should be flexible
	4. Weight: - Material should be light in weight to reduce transportation & handling
	cost.
	5 High resistance to corrosion:-Material should have high resistance to corrosion
	. Brittleness: - Material should not be brittle.
	6 Temperature coefficient of resistance: Material should have low temperature
	coefficient of resistance.
	8 Availability & cost: - Material should be easily available & less costly.
	: Scrap Value: - Material should have high scrap value.
	9
Q. 2 A	Attempt any THREE of the following 12 Marks
	Explain any four advantages of high voltage power transmission.
Ans:	We know that, $P = \sqrt{3} V_L \cos \Box$
	For,
	☐ Same power to be transferred
	At same power factor
	At same transmission line distance
	I $\frac{\Pi}{V}$ from This Equation It is clear that due to High Transmission Voltage
	Following are the advantages Hence EHVAC Transmission is adopted:
	Advantages: (Any Four point expected: 1 Mark each, Total 4 Marks)
	1. As Transmission voltage increases, current decreases. (as $\frac{I}{V}$)
	2. As current decreases, cross section of conductor decreases. [as c/s of conductor $\Box I$] 3. As cross section of conductor decreases, its weight decreases.

SUMMER-2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 5 of 28


- 4. As weight of the conductor decreases, design of tower becomes lighter in weight.
- 5. As current decreases, cross section of bus bar and size of switch gear contact etc. reduces.
- 6. Due to above advantages, Transmission cost per KM decreases
- 7. As transmission voltage increases. A current decreases, so copper losses in transmission line reduces.(as Cu.losses [I2])
- 8. As copper losses reduces, transmission efficiency increases [as Tr. $\Box T \Box \frac{1}{Cu . loss}$]
- 9. As current reduces, voltage drop in transmission line reduces. [as Voltage drop \Box I $\Box \frac{1}{V}$]
- 10. As voltage drop in transmission reduces, voltage regulation becomes better (improved).
- 11. As efficiency and regulation of transmission line gets improved, so performance of transmission line increases
- 12. As transmission voltage increases power handling capacity of transmission line increases (as $P \square V2$)
- 13. Due to high voltage transmission line, successful interconnection of transmission line is possible than low voltage.
- 14. Generating Stations are generally located away from load centre.

 Hence, HVAC transmission line becomes necessary for bulk power to be transmitted over a long distance

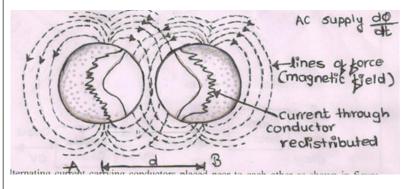b) Describe the proximity effect and state its two disadvantages.

Proximity effect:

(Figure: 1 Mark, Explanation: 2 Mark & disadvantages: 1 mark, Total 4 Marks)



Ans:

Explanation:

Let two alternating current carrying conductors placed near to each other as

SUMMER-2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 6 of 28

shown in figure. Due to electro-magnetic action, flux produced by each conductor links with each other. Due to this super –impose of magnetic field on conductor causes current in each conductor is re-distributed. This is known as proximity effect.

Disadvantages of proximity effect:- (Any Two point expected)

- 1 Current in each conductor is re-distributed
- . That is current is not uniformly distributed through cross section of conductor
- 2 Due to above two reasons Cross section of conductor is not fully utilized.
- . Therefore effective area of conductor reduces so its resistance increases
- 3 (SinceR $\square \square I / A$)

7

8

- Due to increase in resistance, copper losses increases (Since copper losses = I 2R)
- : So transmission efficiency reduces.
- 6 Due to increase in resistance, Voltage drop increases (Since Voltage drop = I R)
- So voltage regulation becomes poor (increases)


www.and.avalaia.Di.nalay.LIV/DC.tyanan

c) Draw and explain Bi-polar HVDC transmission line.

Ans: Bipolar HVDC transmission line (System):

(Figure: 2 Mark & Explanation: 2 Mark, Total 4 Marks)

Layout of Bipolar DC transmission

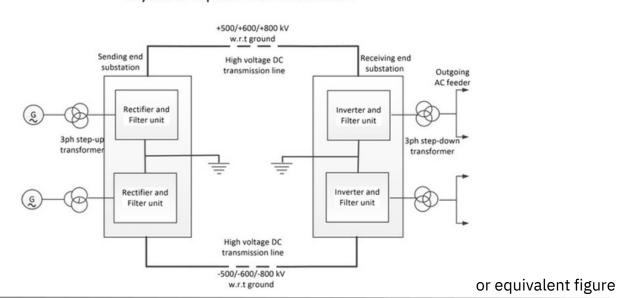

SUMMER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 7 of 28


	Explanation:-
	\Box It has two conductors. One at positive potential & other at negative potential at
	same magnitude w.r.t. ground
	☐ Both conductors operate at equal potential, so current at ground is zero.
d) Ans:	State the different methods of improving string efficiency. Explain any one method in
AII5.	The Methods of Improving String Efficiency:-
	(Methods : 2 Mark & Any one explanation: 2 Marks : Total 4 Marks)
	1) By reducing value of 'm' or ('k') by using longer cross arm.
	2) By Making of 'm' or ('k') equal to zero
	3) By grading of Insulator.
	4) By Using guard ring .
	Explanation:-
	1) By reducing value of 'm' or ('k') by using longer cross arm:-
	Fig:-
	The value of 'm' can be decreased by reducing value of shunt capacitance (C1)
	since $m = C1/C$.
	In order to reduce value shunt capacitance (C1) distance of string of
	insulator from tower must be increased. i.e. by using longer cross arm. Due to this
	value of shunt capacitance (C1) reduces.
	Therefore value of m reduces Since (m \Box $\frac{C}{C}$ 1) As value of 'm' reduces there
	will be more uniform voltage distribution along a string of suspension insulator. In
	this way string efficiency increases.
	Limitation:
	In practice there is limitation to increase length of cross arm as cost o
	tower increases. In practice m= 0.1 is the limit which can be achieved by this
	method.

SUMMER- 2019 Examinations Model Answer

Page 8 of 28

2) By Making of 'm' or ('k') equal to zero:-

Subject Code: 22419

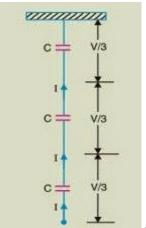

or equivalent Figure

If an insulating material or any non conducting material of high strength is used for connection between two disc insulators in a string instead of using steel part.

Than value of Shunt Capacitance (C1) becomes Zero,(Capacitance will not form) therefore value of 'm' becomes zero (since m = C1/C) So string efficiency becomes 100%.

3) By grading Insulator:-

In this method, disc insulators of different dimensions are so selected that each disc has different capacitance. The assembly in the string of suspension insulator is made in such a way that the top unit insulator has fewer dimensions. (Less capacitance)

(C□A) and dimensions of insulators progressively goes on increasing i.e. bottom unit


In this way it equalizer potential distribution across the string and therefore increase string efficiency.

This method has disadvantages that it requires disc insulator of different dimensions in one string of suspension insulator. Practically it is not possible to obtain such ration. But very high voltage transmission line (1200KV). This method is used.

SUMMER-2019 Examinations

Subject Code: 22419 Model Answer Page 9 of 28

4) By Using guard ring:-

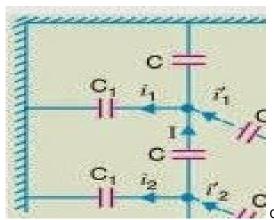

材 or equivalent Figure

Guard ring is a metal ring electrically connected to conductor and surrounding the bottom insulator.

Due to guard ring leakage current through all discs in a string is same.

So, we will get uniform voltage distribution along the string of suspension insulator, In this way string efficiency increases.


Q.3 Attempt any THREE of the following

12 Marks

a) Draw the single line diagram of AC electric transmission and distribution system.

Ans: \$ingle line diagram of AC electric transmission and distribution system: (4 Mark)


Layout of Electric supply System

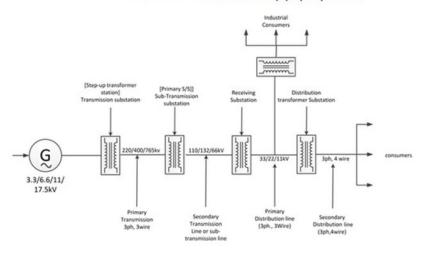

OR

SUMMER- 2019 Examinations

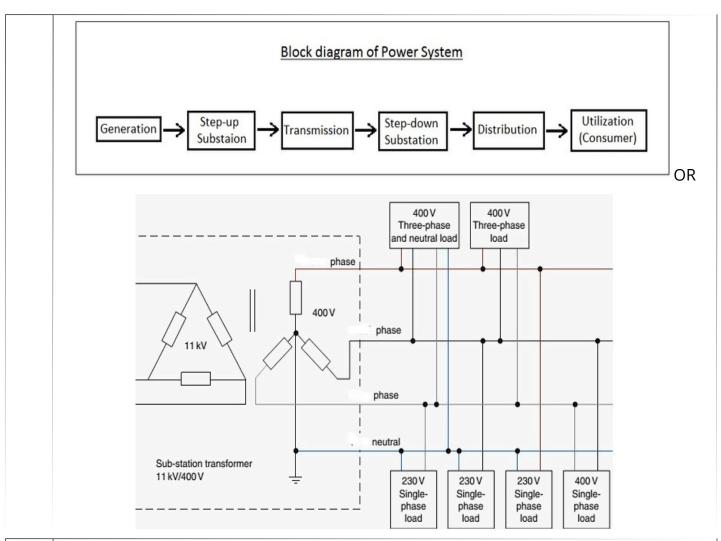Subject Code: 22419 <u>Model Answer</u> Page 10 of 28



b) | Explain the Ferrantio effect in detail.

Ans: Under Following conditions Ferranti effect occurs:

(Any Two condition expected: 1 Mark each: Total: 2 Marks)

- 1. When there is no load on transmission line (I = 0) OR
- 2. When There is no load at receiving sub-station or Lightly loaded OR
- 3. When there is sudden load thrown OFF. OR
- 4. When there is sudden load shading. OR
- 5. When Transmission line is open circuited due to load failure.

SUMMER-2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 11 of 28

Ferranti effect : (2 Marks)

Under any one above condition, it is observe that receiving end voltage (VR) is found to be greater than sending end voltage (VS). This phenomenon is known as Ferranti effect.

c) Explain the grid system of distribution and state its advantages.


Ans: Grid distribution system:-

(2 Marks)


In this system, when the feeder or loop or ring is charged (energized) by two or more than two substations from two or more than two different generating stations then it is known as "Grid distribution system. In this system only one feeder is utilized at a time.

Layout of Grid distribution scheme:

(1 Marks)

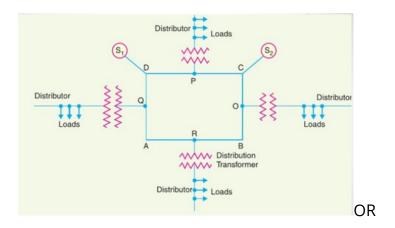

Grid distribution system

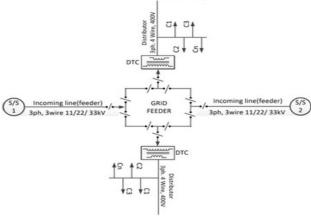

or equivalent figure

SUMMER-2019 Examinations


Subject Code: 22419 <u>Model Answer</u> Page 12 of 28

Advantages of Grid distribution scheme:


(Any Two point expected: 1/2 Mark each: Total 1 Mark)

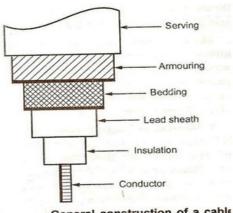- 1. Supply to distribution transformer center is given through two different generating stations or major generating stations
- 2. It has highest reliability to maintain supply even when there is a fault on any one feeder
- 3. It has highest reliability to maintain supply even when there was maintenance on any one feeder.
- d) Draw and explain the construction of underground cables.

Ans: Underground cables: (Diagram : 2 Mark & Explanation: 2 Mark, Total 4 Marks)



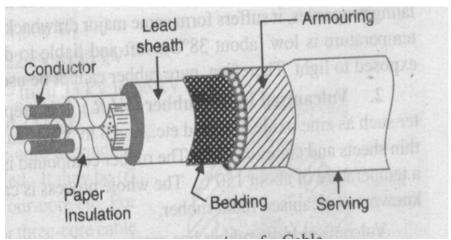General construction of a cable or equivalent figure OR



or equivalent

figure

SUMMER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 13 of 28

Evnlanat	tion:-			
i) Core or conductor:				
	It function is carry current.			
	Cable may have single or more than single core conductor.			
	Conductor are made up of copper or aluminium material			
	Cross section of conductor is directly proportional to current. (Cross section of			
	conductor depends upon current carrying capacity)			
	Conductor used is -			
	☐ Annealed			
	□ Tinned			
ii) Insu	ılation:			
	Each core of conductor is provided with suitable thickness of insulation to avoid			
	short circuit between two conductors.			
	The thickness of insulation layer depends on magnitude of voltage for which it			
	is designed.			
	Commonly used materials for insulation are e.g.:-			
	☐ PVC (Polyvinyl Chloride)			
	☐ Polyethene			
	XLPE (Cross- linked polyethylene)			
iii) Lead	(Metallic) Sheath:			
	It is provided over insulation.			
П	To provide the protection of core from entry of moisture, gases or other			
	damaging liquids (acids & alkaline) in the soil & atmospheric.			
П	The metallic sheath is made up of lead or lead alloys recently aluminum is also			
Ц	being used as a metallic sheath.			
iv) Bed				
	Over the metallic sheath there is layer of bedding.			
	The function of bedding is protecting the metallic sheath against corrosion &			

SUMMER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 14 of 28

		from the mechanical injury due to armouring.	
		It is made from fibrous material such as jute, hessian tape	е
	v) Armo	uring:	
		This layer is over a bedding only for underground cable an	nd not for over head
		cable	
		Its function is to protect the cable from mechanical injury	
		It covers the bedding, which consists of 1 or 2 layers of ga	alvanized steel wire or
		steel tapes	
	vi) Ser	ving:	
		This layer is last layer which comes over armouring.	
		Its function is to protect armouring against rusting and it a	also helps for easy
		handling of cables.	
		It is similar to bedding & consists of fiborous material suc	h as jute.
Q.4	Attempt	any THREE of the following	12 Marks
		classification of transmission lines based on voltage leve	
		<u> </u>	er and length of lines.
Ans:		ding to Voltage level:	(2 Marks)
	A) Accor		
	A) Accor	ding to Voltage level:	(2 Marks)
	A) Accorda a) b)	ding to Voltage level:) High voltage Transmission Line (HV) up to 33 KV	(2 Marks)
	A) Accordal a) b) c)	ding to Voltage level:) High voltage Transmission Line (HV) up to 33 KV) Extra High Voltage Transmission Line (EHV) above 33 KV up to 40	(2 Marks)
	A) Accordate A)	ding to Voltage level:) High voltage Transmission Line (HV) up to 33 KV) Extra High Voltage Transmission Line (EHV) above 33 KV up to 40) Ultra High voltage Transmission Line (UHV) above 400 KV	(2 Marks) 00 KV
	A) Accordate A) Accordate A) Accordate A) Accordate A) S	ding to Voltage level:) High voltage Transmission Line (HV) up to 33 KV) Extra High Voltage Transmission Line (EHV) above 33 KV up to 40) Ultra High voltage Transmission Line (UHV) above 400 KV ding to Length of Transmission line:	(2 Marks) 00 KV
	A) Accordal by C) B) Accordal a) S b) N	ding to Voltage level: High voltage Transmission Line (HV) up to 33 KV Extra High Voltage Transmission Line (EHV) above 33 KV up to 40 Ultra High voltage Transmission Line (UHV) above 400 KV ding to Length of Transmission line: Short Distance Transmission Line - (up to 50 KM)	(2 Marks) 00 KV
	A) Accordal by C) B) Accordal a) S b) N	ding to Voltage level: High voltage Transmission Line (HV) up to 33 KV Extra High Voltage Transmission Line (EHV) above 33 KV up to 40 Ultra High voltage Transmission Line (UHV) above 400 KV ding to Length of Transmission line: Short Distance Transmission Line - (up to 50 KM) Medium Distance Transmission Line - (up to 50 to 150 KM)	(2 Marks) 00 KV
	A) Accordal by c) B) Accordal s b) N c) L	ding to Voltage level: High voltage Transmission Line (HV) up to 33 KV Extra High Voltage Transmission Line (EHV) above 33 KV up to 40 Ultra High voltage Transmission Line (UHV) above 400 KV ding to Length of Transmission line: Short Distance Transmission Line - (up to 50 KM) Medium Distance Transmission Line - (up to 50 to 150 KM) ong Distance Transmission Line - (above 150 KM)	(2 Marks)
	A) Accordal a) b) c) B) Accordal a) S b) N c) L	ding to Voltage level: High voltage Transmission Line (HV) up to 33 KV Extra High Voltage Transmission Line (EHV) above 33 KV up to 40 Ultra High voltage Transmission Line (UHV) above 400 KV ding to Length of Transmission line: Short Distance Transmission Line - (up to 50 KM) Medium Distance Transmission Line - (up to 50 to 150 KM) ong Distance Transmission Line - (above 150 KM) OR Transmission Line: - The length of Short transmission Line	(2 Marks)
	A) Accordal, b) c) B) Accordal a) S b) N c) L	ding to Voltage level: High voltage Transmission Line (HV) up to 33 KV Extra High Voltage Transmission Line (EHV) above 33 KV up to 40 Ultra High voltage Transmission Line (UHV) above 400 KV ding to Length of Transmission line: Short Distance Transmission Line - (up to 50 KM) Medium Distance Transmission Line - (up to 50 to 150 KM) ong Distance Transmission Line - (above 150 KM) OR	(2 Marks) (2 Marks) (2 Marks) ne is up to 50KM and

SUMMER-2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 15 of 28

and its line voltage is between 20KV to 100 KV 50KM- 150KM


3) Long Transmission Line: - The length of Long transmission Line is above 150KM and its line voltage is above 100K

OR

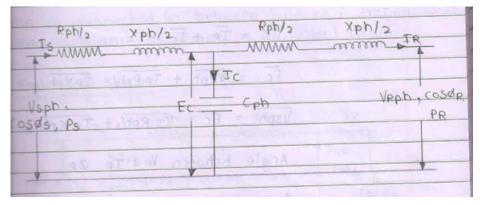
- 1) Short Transmission Line: The length of Short transmission Line is up to 80KM and its line voltage is less than 20 KV
- 2) Medium Transmission Line: The length of Medium transmission Line is up to 80KM- 200KM and its line voltage is between 20KV to 100 KV
- 3) Long Transmission Line: The length of Long transmission Line is above 200KM and its line voltage is above 100KV
- b) Draw the circuit diagram and phasor diagram of nominal T method of medium transmission line.

Circuit Diagram:-

(Diagram: 2 Mark & Vector diagram: 2 Mark: Total 4 Marks)




OR

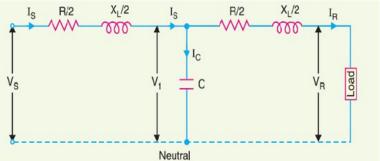

or equivalent figure

SUMMER-2019 Examinations

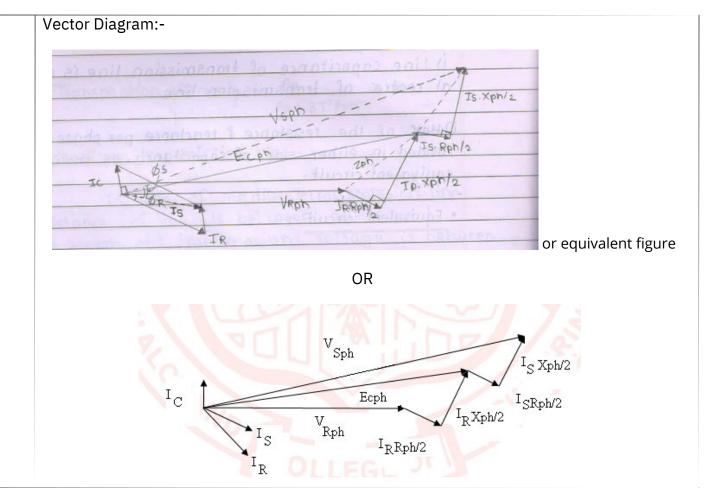Subject Code: 22419 <u>Model Answer</u> Page 16 of 28



c) \$tate the limitations of EHVAC transmission line.

Ans: Following are the Limitations of EHVAC Transmission:

(Any four point expected: 1 each point, Total 4 Marks)

- 1. Insulation cost increases as voltage increases
- 2. Skin effect is more
- 3. Proximity effect is more.
- 4. Corona loss increases.
- 5. Radio interference increases
- 6. String efficiency is less than 100%
- 7. Ground return not possible.
- 8. Voltage control is not easily possible.
- 9. Power flow cannot be easily controlled.
- 10 Short circuit current level is more

_

SUMMER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 17 of 28


11. In case of EHVAC, Intermediate substation is required at every 250 km to improve the performance of transmission line If power is to be transmitted of EHVAC through

- 12. underground cable then there is limitation on the length of cable due to charging current. e.g. for 400 KV line limitation on length of cable is 25 Km Asynchronous tie not possible. Stability of EHVAC is very low because of presence of inductance.
- Transient performance is poor. There is limitation on power transfer due to presence of inductance of

14

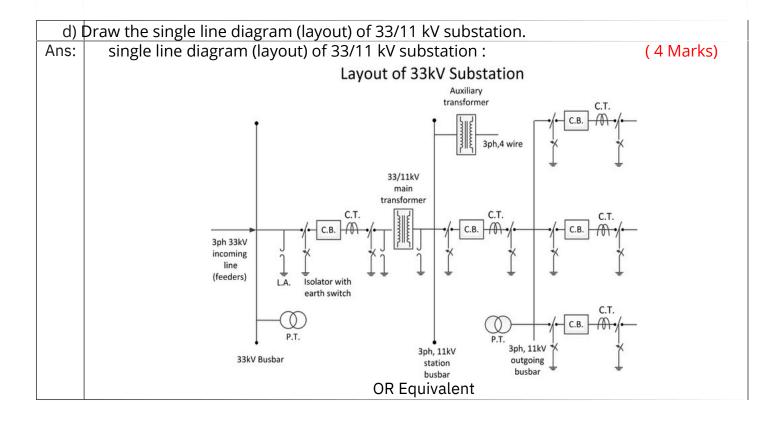16.

- transmission line & power angle.
- 17. To improve the performance of transmission line additional equipments such as series & shunt reactor & capacitor are required which increases cost of substation.
- 18. EHVAC is economical only for bulk amount of power is to be transmitted over long distance.




SUMMER-2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 18 of 28

e) Explain the shackle type insulator with neat sketch.

Ans: | Shackle type insulator with neat sketch:

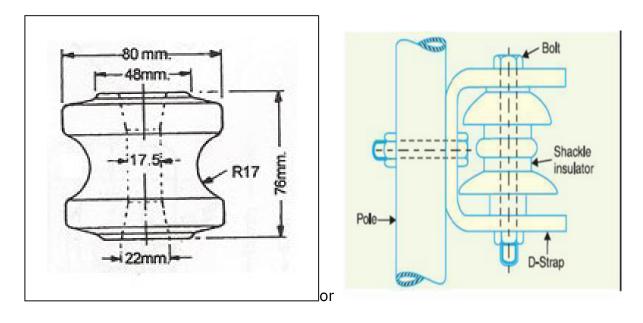(Figure: 2 Mark, Explanation: 2 Marks, Total: 4 Marks)



Explanation:

- ☐ These insulators are clamped to the cross arms by one metal 'U' clamp with the help of bolts, nuts & washers.
- ☐ Function of Shackle insulator is <u>to reduce excessive tension on line.</u> Also on supporting structure (pole).

Applications:

- 1) Shackle insulators are used in following circumstances when line is subjected excessive tension. E.g. shackle insulators are used below 11 KV line & above 11 KV line strain insulators are used
 - 2) Shackle insulators are also used when line is going straight but in case of vertical conductor configuration only

SUMMER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 19 of 28

0.5	TANK CIT CIT I
Q.5	Attempt any TWO of the following 12 Marks
a)	Discuss the effect of transmission line parameters on the performance of transmission line (any six points).
Ans:	Following are the effect on performance of transmission line:
	(Any Six point expected: 1 Marks each, Total 6 Marks)
	1.Due to resistance (R), voltage drop in transmission line produces
	2.Due to resistance (R), copper losses in transmission line produces.
	3.Due to inductance (L) voltage drop in transmission line produces.
	4.Capacitor (C) draws charging current through transmission line. This charging
	current produces additional copper losses & voltage drop in transmission line.
	5.Due to above reasons, transmission line efficiency gets affected
	6. voltage regulation of transmission line gets affected
	7.Also power factor of transmission line gets affected
	Explain the features of flexible AC transmission line (any four). State types of FACTS controller.
b) Ans:	
	4 Mark & Types: 2 Mark, Total 6 Marks)
	1 FACTS increase the reliability of AC grids.
	. It controls the voltage under various load condition
	2 It balance reactive power (both lagging and leading reactive power)
	. It improves power quality
	3 It increases transmission efficiency
	. It also help to solve technical problems in the interconnected power system.
	4 They reduce power delivery costs.
	. There is fast voltage regulation.
1	

.


SUMMER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 20 of 28

10. Better utilization of the network, 11. Increased availability and reliability 12. As well as improved network stability are achieved along with higher supply quality. OR In conventional AC transmission system the ability to transfer AC power is limited due to various reasons. So the actual amount of power transferred to the load (active power) is always less than apparent power. For ideal transmission, the active power should be equal to apparent power. The main purpose of facts to obtain active power nearly equal to apparent power by supplying lagging reactive power or leading reactive power as per requirements. For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS for series compensation:- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) Static VAR compensator (SVC) #Single phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm pe kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		9. Increased power transfer over long AC lines.
12. As well as improved network stability are achieved along with higher supply quality. OR ☐ In conventional AC transmission system the ability to transfer AC power is limited due to various reasons. ☐ So the actual amount of power transferred to the load (active power) is always less than apparent power. ☐ For ideal transmission, the active power should be equal to apparent power. ☐ The main purpose of facts to obtain active power nearly equal to apparent power by supplying lagging reactive power or leading reactive power as per requirements. ☐ For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) 3. Static VAR compensator (SVC) Resingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load power factors refer to the load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm pet kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		10. Better utilization of the network,
OR ☐ In conventional AC transmission system the ability to transfer AC power is limited due to various reasons. ☐ So the actual amount of power transferred to the load (active power) is always less than apparent power. ☐ For ideal transmission, the active power should be equal to apparent power. ☐ The main purpose of facts to obtain active power nearly equal to apparent power by supplying lagging reactive power or leading reactive power as per requirements. ☐ For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) 3. Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load power factors refer to the load power factors refer to the voltage at the far end.		11. Increased availability and reliability
OR □ In conventional AC transmission system the ability to transfer AC power is limited due to various reasons. □ So the actual amount of power transferred to the load (active power) is always less than apparent power. □ For ideal transmission, the active power should be equal to apparent power. □ The main purpose of facts to obtain active power nearly equal to apparent power by supplying lagging reactive power or leading reactive power as per requirements. □ For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) . Static VAR compensator (SVC) ### Single phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm pe kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		12. As well as improved network stability are achieved along with higher supply
□ In conventional AC transmission system the ability to transfer AC power is limited due to various reasons. □ So the actual amount of power transferred to the load (active power) is always less than apparent power. □ For ideal transmission, the active power should be equal to apparent power. □ The main purpose of facts to obtain active power nearly equal to apparent power by supplying lagging reactive power or leading reactive power as per requirements. □ For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) 3. Static VAR compensator (SVC) ### Single phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm pe kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		quality.
due to various reasons. So the actual amount of power transferred to the load (active power) is always less than apparent power. For ideal transmission, the active power should be equal to apparent power. The main purpose of facts to obtain active power nearly equal to apparent power by supplying lagging reactive power or leading reactive power as per requirements. For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		OR
□ So the actual amount of power transferred to the load (active power) is always less than apparent power. □ For ideal transmission, the active power should be equal to apparent power. □ The main purpose of facts to obtain active power nearly equal to apparent power by supplying lagging reactive power or leading reactive power as per requirements. □ For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) . Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor. In load power factors refer to the voltage at the far end.		$\hfill \square$ In conventional AC transmission system the ability to transfer AC power is limited
than apparent power. For ideal transmission, the active power should be equal to apparent power. The main purpose of facts to obtain active power nearly equal to apparent power by supplying lagging reactive power or leading reactive power as per requirements. For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation:- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		due to various reasons.
□ For ideal transmission, the active power should be equal to apparent power. □ The main purpose of facts to obtain active power nearly equal to apparent power by supplying lagging reactive power or leading reactive power as per requirements. □ For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) 2. Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		$\ \square$ So the actual amount of power transferred to the load (active power) is always less
□ The main purpose of facts to obtain active power nearly equal to apparent power by supplying lagging reactive power or leading reactive power as per requirements. □ For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) . Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		than apparent power.
by supplying lagging reactive power or leading reactive power as per requirements. For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		☐ For ideal transmission, the active power should be equal to apparent power.
requirements. For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) 2. Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		☐ The main purpose of facts to obtain active power nearly equal to apparent power
For this, FACTS uses static power electronics devices for series & shunt compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) 2. Static VAR compensator (STATCOM) 3. Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		by supplying lagging reactive power or leading reactive power as per
compensation automatically as per requirements. Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1 Static synchronous compensator (STATCOM) . Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		requirements.
Types of FACTS controller:- Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) 2. Static VAR compensator (STATCOM) 3. Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		$_{\square}$ For this, FACTS uses static power electronics devices for series & shunt
Examples of FACTS for series compensation :- (Any one types expected) 1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) 2. Static VAR compensator (STATCOM) 3. Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		compensation automatically as per requirements.
1. Thyristor-controlled series reactor (TCSR) 2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1. Static synchronous compensator (STATCOM) 2. Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		Types of FACTS controller:-
2. Thyristor-controlled series capacitor (TCSC) Examples of FACTS for shunt compensation:- (Any one types expected) 1 Static synchronous compensator (STATCOM) . Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		Examples of FACTS for series compensation :- (Any one types expected)
Examples of FACTS for shunt compensation:- (Any one types expected) 1 Static synchronous compensator (STATCOM) . Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		1. Thyristor-controlled series reactor (TCSR)
 Static synchronous compensator (STATCOM) Static VAR compensator (SVC) Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end. 		2. Thyristor-controlled series capacitor (TCSC)
Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		Examples of FACTS for shunt compensation:- (Any one types expected)
Asingle phase AC distributor AB 300 M long is fed from end A and is loaded as under (i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from c) point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		1 Static synchronous compensator (STATCOM)
(i) 100 A at 0.707 pf lagging 200 m from point A. (ii) 200 A at 0.8 pf lagging 300 m from c) point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm per kilometer. Calculate total voltage drop in the distributor. The load power factors refer to the voltage at the far end.		. Static VAR compensator (SVC)
Ans: Given data:	C)	(i) 100 Å at 0.707 pf lagging 200 m from point A. (ii) 200 Å at 0.8 pf lagging 300 m from point A, The load resistance and reactance of the distributor is 0.2 ohm and 0.1 ohm pekilometer. Calculate total voltage drop in the distributor. The load power factors refer t
	Ans:	Given data:

SUMMER-2019 Examinations

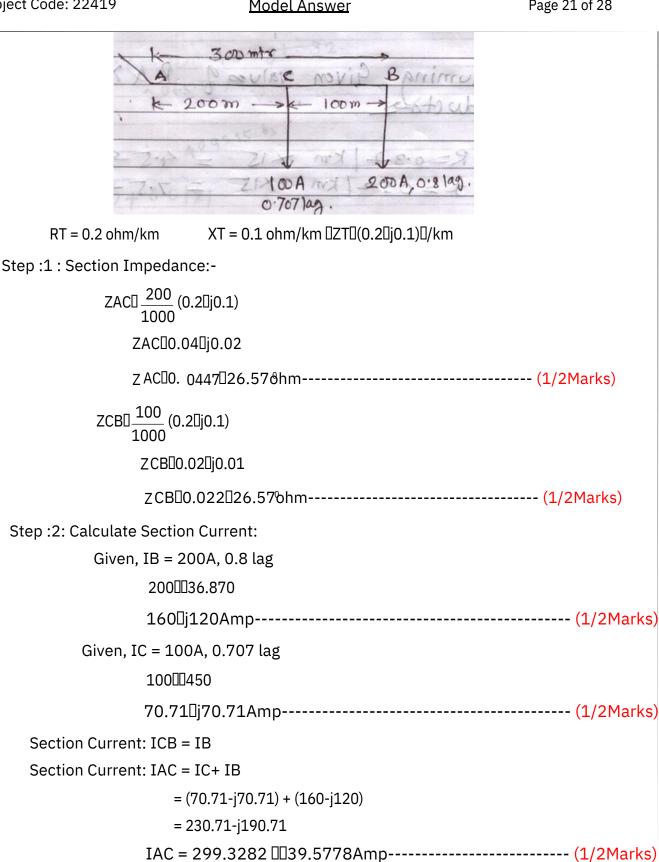Subject Code: 22419 **Model Answer** Page 21 of 28



SUMMER- 2019 Examinations

	SUMMER - 2019 Examinations	
Su	ubject Code: 22419 Model Answer	Page 22 of 28
	Step :3: Calculate Voltage drop in section AC:-	
	VACIIACIZAC	· (1/2Marks)
	\[\(\(\(\text{299.3282\text{1}\text{39.5778}} \) \(\(\(\text{0.0447\text{1}\text{2}6.57} \) \)	
	□13.37997054 □ □13.0078V	
	□13.0366 □ j 3.01161V	(1/2 Mark)
	Calculate Voltage drop in section BC:-	(=/=:::::)
	= ICB X ZCB	(1/2Marks
	= (2000036.87)(0.02236026.565)	
	50	
	= 4.48□□10.3 Volts	
	VBC = 4.407[j0.80 Volts	(1/2Marks)
	Step 4: Calculate total voltage drop in distributor VAB :-	
	Voltage drop in section BC + Voltage drop in	n section AC
	□(4.407□ j0.80)□(13.0366□ j3.01161)	
	□17.9936□j3.8116Volt	(1 Mark)
	V AB [17.8552] [12.359 Volt	(211611)
	Step 5: Calculate Load power factor :-	
	□Cos(12.3259)	
		(1/2Marks)
	=0770 xagging	(1/21 lai 10)
Q.6	Attempt any TWO of the following	12 Marks
	A 3 phase line of 4 km length delivers 4000 kW at a p.f	of 0.8 lagging to a load the
a)	resistance and reactance per km of each conductor are 0.2 if the voltage at the supply end is maintained at 11 kV. Calcu	ohm and 0.5 ohm respective that the received end
	voltage and efficiency of line.	
Ans:	$P_{R} = 4000 \text{ KW} = 4000 \times 10^{3} \text{W}$, $VR = 11 \text{ KV} = 11 \times 10^{-3} \text{V}$, $P.F. = 0.8 \text{ lag}$,	R Per conductor =0.2 ohm, X
	Per conductor = 0.5 ohm	
	110103	,
	$VRph = VRPh \begin{bmatrix} \frac{110103}{\sqrt{3}} & VR_{ph} \end{bmatrix} $	V
	To Calculate Total /loop values of R & X	
	Total resistance RT = 4 R= 0.2 4= 0.8 ohm	
	Total Reactance XT = 4 X =0.5 4= 2 ohm Step 1: To calculate cu	rrent:
	Power P = VIcos[]	

(ISO/IEC-27001-2005 Certified

SUMMER-2019 Examinations Subject Code: 22419 Model Answer Page 23 of 28 $I \; \square \; \frac{P}{\sqrt{3} \; V_L \; cos \square} \; , \quad I \; \square \; \frac{4000 \square 10^3}{\sqrt{3} \; \square 1 \square 10^{-3} \; \square 0.8}$ -----(1 Mark) II262.4319amp Step 2: To calculate Total Line Losses: Total Line Losses = 3I2RPh $= 3(262.4319)2 \square 0.8$ = 16289.2051 Watt -----(1 Mark) Step 3: To calculate Total Transmission efficiency: $\% \square T \square \frac{4000 \square 103}{4000 \square 103 \square 165289.2051} \square 100$ Ø0[T] 69.0317/₀ -----(1 Mark) Step 6:To calculate % regulation: % Voltage Regulation = $\frac{I (R ph Cos \square R \square X_{ph} Sin \square R}{I (R ph Cos \square R \square X_{ph} Sin \square R} \square 100 ----- (1/2 Mark)$ $= \frac{262.4319(0.8 \square 0.8 \square 2 \square .6)}{6.3508 \square 10^{3}} \square 100$ = 7.6034 % -----(1 Mark) Step 3: To calculate Sending end voltage: VSph= \ROIDRRPhcosOROXPhsinORO -----(-1/2 Mark)----= 6.3508[103[262.74[0.8[0.8[2]0.6]] $= 6.3508 \Pi 103 \Pi 483.4416$ VSPh = 6833.6747 volt $VSL = 6833.6747 \times \sqrt{3}$ -----(1/2 Mark) VSL= 11836.2718 volt

SUMMER- 2019 Examinations


Su	ıbject Code: 22419	<u>Model Answer</u>	Page 24 of 28					
b)	across the line unit is	17.5 kV, calculate the line	g of 3 similar insulators. If the voltage to neutral voltage. Assume that the					
	100011	capacitance between each insulator and earth is 1/8th of the capacitance of insulator						
Ans:	Xlsอ นีเกิดโหฟ string effic	iency.						
	i) Ratio of capacitance 'r	n' :-						
		$m = \frac{1}{8} \Box 0.125$						
		k = m = 0.125	(1 Mark)					
	ii) V 3 = V1 (1 +3m +m) ²							
	V3 🛮 V1 (1 🗓 3 🗷 0.125 🖟 (0.125)2)							
	17.501.3906 V ₁							
	$V1 = \frac{17.5}{1.390625}$							
	V1 = 12.58426966	KV						
			(1 Mark)					
	ii) V20V1(10m)							
	V20V1(100.125)							
	V2 = 12.5842696	6 x 1.125						
	V2 = 14.1573	0337						
			(1 Mark)					
	iii) Voltage across string = Vph = V1 +V2+ V3							
		= 12.58426966 +14.15730337	+17.5					
	VPh:	= 44.24157336 KV						
			(1 Mark)					

SUMMER- 2019 Examinations

Subject Code: 22419	<u>Model</u> /	<u>Answer</u>		Page 25 of 2
vi) String efficiency :	-			
St	ring $\square \% \square \frac{Vph}{\square \square V3} \square 100$			(1 Mark
Str	ing $\square\%\squarerac{10.1036}{3017.5}$ 0100	0		
Sti	ing 🛮 00 🗸 🖂 100 🗸 🗸 100 🗸 100 100 100 100 100 100 100 100 100 10			
				(1 Mar
) Draw the symbols and	d state their function	of comp	onents us	ed in substation (any s
: Symbols in Sub- Stat (Any six symbol fron expected: 1 Mark each	n following are equiva	alent : 1/	2 Mark & th	neir function 1/2 Mark
• Symboles (in sls)	stro.	10000	(a) Distriction Concessor
	also bridge chain			
	r- machania	Serial S		→ · · · · · · · · · · · · · · · · · · ·
The Armer of	G			
The sale Years		Curre	nt Transfe	ormer-himmandhenneft
22.0	I line has span-		THE REAL PROPERTY.	\bigcap
2> Bus Bar-	Aprilla Photos		THE PART	
White Land College to Street To 190	Be solution also	Potenti	ol Tronsp	ormer-
3> Step-up tron	2801W= (20)=			Anthone 8 4 101
Jrep up mi	9,0111101 (30)			
p. 19257 (Circuit	Breaker-	AND THE REAL PROPERTY.
The second	9 1	S CALERY	(along close)	
	so a la long man			01 01 61
Circuit breaker	with isolator.	201		
12-11-11-12 ALC	Alies Astains	(2)		
Manager Const.	-			
The state of the s				
Isolator or group				
Switch (GSO)				
Edouble k				

SUMMER- 2019 Examinations

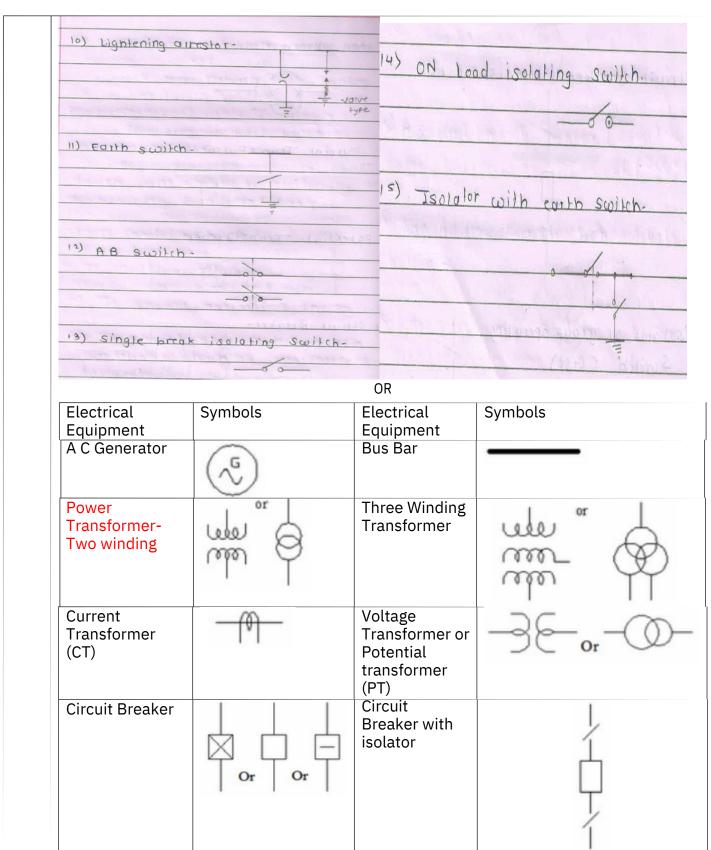Subject Code: 22419 <u>Model Answer</u> Page 26 of 28



SUMMER-2019 Examinations

Subject Code: 22419 Page 27 of 28

Model Answer

Isolator or Group Operating Switch (GOS)	1	Lightening Arrestor (L.A)	OR
Earth Switch (ES)	-\- n	Wave or Line trap	
Coupling Capacitor (CC)	HHI	A B Switch	
			—0 0—

List of the equipment's, circuit elements in substation & their function:

1) Bus bar: -

Bus bar is common conductor to which incoming & outgoing lines are connected

2) Power Transformer (Main transformer) :-

Its function is to step down the incoming voltage (e.g.33 KV) to outgoing voltage (22/11KV) without change in frequency. Its rating is in MVA.

It is installed on strong concrete foundation (plinth). It is oil cooled also air blast cooling system is provided.

3) Auxiliary Transformer (Station transformer): -

Its function is to step down the input voltage (11 KV) to distribution voltage (3-ph, 4wire, 400V) to give supply to control room, area lighting, staff quarters etc,

4) Lightning Arrester: -

It is provided for protection of substation, transformer against lightning stroke .It is connected in between line and ground at the starting point of substation. Under normal condition it acts as an insulator.

SUMMER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 28 of 28

5) Earth switch: -

Its function is to discharge the ground capacitance when line is open circuited for maintenance purpose by isolator.

6) Isolator (No load Switch): -

Its function is to connect or disconnect the circuit only when there is no load.

- 7) Circuit Breaker: It is protective device. It open or break the circuit whenever there is fault & protect the equipment. It can be operated manually or remote control whenever required.
- 8) Relay:

It sense the faults & gives signal to trip circuit of C.B. to open. There are different types of relay e.g. Earth fault relay, Phase to Phase fault relay, Thermal relay etc.

9) Instrumental Transformer (CT & PT):-

C.T & P.T are used for measurement of electrical quantities (Current, voltage, power & energy) also C.T. is used for protection purpose as a part of tripping circuit of C.B.

10) Horn Gap Fuse: -

It is provided to primary side of transformer for protection against over current. (Its frame shape is like a Horn gap due to which arc /spark will extinguish quickly) If C.B. is installed on primary side of transformer than Horn gap fuse is not provided.

ENIF	
ENL	J

22419

11920 3 Hours / 70 Marks

Seat No.								
----------	--	--	--	--	--	--	--	--

Instructions –

- (1) All Questions are Compulsory.
- (2) Illustrate your answers with neat sketches wherever necessary.
- (3) Figures to the right indicate full marks.
- (4) Assume suitable data, if necessary.
- (5) Attempt answers in sequential order, preferably.
- (6) Mobile Phone, Pager and any other Electronic Communication devices are not permissible in Examination Hall.

Marks

1. Attempt any FIVE of the following:

10

- a) State the meaning of Single line diagram
- b) State the classification of transmission lines depending on length of transmission lines.
- c) State the type of distribution substation.
- d) List different transmission line components used for power transmission. (any four)
- e) State features of wireless power transmission.
- f) State line parameters of transmission line.
- g) Define voltage regulation and Transmission Efficiency.

22419 [2]

		Marks			
2.	Attempt any TH <u>REE of t</u> he following:	12			
	a) Differentiate between overhead transmission and underground transmission.				
	b) Draw the layout of Homopolar transmission line.				
	c) State the advantages of use of high voltage in transmission of Electric power.				
	d) Draw the layout of power system indicating Generation, Transmission and distribution parts.				
3.	Attempt any TH <u>REE of t</u> he following:	12			
	a) Draw the diagram representing transposition of conductor and state its importance.				
	b) State the standard voltage in India for Generation, transmission distribution system.				
	c) List the factors to be considered while designing feeders and distribution with their functions in brief.				
	d) State advantages and disadvantages of radial distributor system.				
4.	Attempt any TH <u>REE of t</u> he following:	12			
	a) List classification of distributor system with their advantages each. (any two)				
	b) A 3-φ overhead line supported by 6 disc insulators, the potential across the unit is 11 KV. Assuming shunt capacitance between each Insulator and each metal link is of 1/5th of capacitance of insulator. Calculate:				
	(i) line voltage				
	(ii) string efficiency.				
	c) State the meaning of skin effect and how can it be minimised.				
	d) Draw the diagram of pin type and suspension type insulators.				
	e) State the effects of low power factor on efficiency and voltage regulation of short transmission lines.				
	f) State the condition for selecting site for distribution substation.				

22419 [3]

				Marks	
5.	A	Attem	pt any TW <u>O of t</u> he following:	12	
	a) [equation for string efficiency with 3 - disc insulators spension type.		
	b) [Corona, List its causes and state how can it be avoided. each)		
	c) S	State t	he meaning of ferranti effect and proximity effect.		
6.	A	Attem	pt any TW <u>O of t</u> he following:	12	
	a) Compare nominal - I and nominal - II method of transmission line (Any six points)				
	b) State the meaning of FACTS and explain in brief d-types facts controller.				
	c)	(i)	List the properties of line insulators in brief.		
		(ii)	List the methods of Line Support Erection and explain in brief any one.		

WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 1 of 27

Important suggestions to examiners:

- 1) The answers should be examined by key words and not as word-to-word as given in the model answer scheme.
- 2) The model answer and the answer written by candidate may vary but the examiner may try to assess the understanding level of the candidate.
- 3) The language errors such as grammatical, spelling errors should not be given more importance. (Not applicable for subject English and communication skills)
- 4) While assessing figures, examiner may give credit for principle components indicated in a figure. The figures drawn by candidate and model answer may vary. The examiner may give credit for any equivalent figure drawn.
- 5) Credits may be given step wise for numerical problems. In some cases, the assumed constant values may vary and there may be some difference in the candidate's answers and model answer.
- 6) In case some questions credit may be given by judgment on part of examiner of relevant answer based on candidate understands.
- 7) For programming language papers, credit may be given to any other program based on equivalent concept.

Q.1	Attempt any FIVE of the following	10 Marks
a) :	State the meaning of Single line diagram	
Ans:	Meaning ofSingle line diagram: (Or equivalent)	(2 Marks)
	The single line diagram of a power system is the network which shows connections and arrangement of the system components along with t as output rating, voltage, resistance and reactance, etc.).	
	OR	
	In power engineering, a one-line diagram or single-line diagram (SLD) simplified notation for representing a three-phase power system. Electure such as circuit breakers, transformers, capacitors, bus bars, and conditions shown by standardized schematic symbols.	ctrical elements uctors are
b)	State the classification of transmission lines depending on length lines.	of transmission
Ans:	According to Length of Transmission line:	(2 Marks)
	a) Short Distance Transmission Line - (up to 50 KM)	
	b) Medium Distance Transmission Line - (up to 50 to 150 KM)	
	c) Long Distance Transmission Line - (above 150 KM)	

WINTER- 2019 Examinations

Subject Code: 22419 Page 2 of 27

Model Answer

OR

- 1) Short Transmission Line: The length of Short transmission Line is up to 50KM and its line voltage is less than 20 KV
- 2) Medium Transmission Line: The length of Medium transmission Line is up to 50KM- 150KM and its line voltage is between 20KV to 100 KV
- 3) Long Transmission Line: The length of Long transmission Line is above 150KM and its line voltage is above 100K

OR

- Short Transmission Line: The length of Short transmission Line is up to 80KM and its line voltage is less than 20 KV
- 2) Medium Transmission Line: The length of Medium transmission Line is up to 80KM- 200KM and its line voltage is between 20KV to 100 KV
- 3) Long Transmission Line: The length of Long transmission Line is above 200KM and its line voltage is above 100KV
- c) State the type of distribution substation.

Ans: The classification of distribution substation.

(Any Four point expected: 1/2 Mark each, Total 2 Marks)

- 1 Pole mounted distribution substation
- . Plinth mounted distribution substation
- 2 Compact/prefabricated distribution substation
- · Underground distribution substation
- 3 Indoor distribution substationOutdoor distribution substation
- 4 Mobile distribution substation

5

.

6

_

7

WINTER- 2019 Examinations

Subject Code: 22419 Model Answer Page 3 of 27

d) List different transmission line components used for power transmission. (any four) Following are the Transmission line components used for power transmission line:-Ans:

(Any Four components are expected: 1/2 Mark each, Total 2 Marks)

- 1. Supporting structure (pole)
- 2. Line insulator
- 3. Overhead conductor
- 4. 'V' Cross arm
- 5. Top pin support
- 6. Two Pin Cross arm
- 7. Four pin cross arm
- 8. Stay set (Stay wire of 7/8 or 7/10 SWG)
- 9. Lighting arrestors
- 10. Guarding wires
- 11. Continuous earth wire
- 12. Cables
- 13. Fuses and Isolating switches
- 14. Different types of fabrication Clamp (A-type, B-Type)
- 15. Bird guards
- 16. Vibration damper
- 17. Jumpers

e) S	State	features	of wireless	power	transmission.

Ans:

Features of wireless power transmission:

(Any four point expected: 1/2 Mark each, Total 2 Marks)

- 1. Energy delivered anywhere in the world
- 2. Zero fuel cost

WINTER-2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 4 of 27

- 3. Less losses
- 4. Less use of copper wires
- 5. More efficiency
- 6. Minimum long-range environmental impact

OR

Features of wireless power transmission:

(Any Four point expected: 1/2 Mark each, Total 2 Marks)

- An electrical distribution system, based on this method would eliminate the need for an inefficient, costly, and capital intensive grid of cables, towers, and substations.
- 2. It will rid the landscape of wires, cables, and transmitting towers.
- 3. The electrical energy can be economically transmitted without wires to any terrestrial distance, so there will be no transmission and distribution loss.
- 4. More efficient energy distribution systems and sources are needed by both developed and under developed nations.
- 5. To transmit wireless power to any distance without limit. It makes no difference what the distance is.
- 6. The power failure due to short circuit and fault on cables would never exist in the transmission.
- 7. Power theft would be not possible at all.

f) \$tate line parameters of transmission line. Ans: Following are the of Line parameters of transmission line: (2 Marks) 1. Resistance 2. Inductance 3. Capacitance

WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 5 of 27

g)	Define voltage regulation and Transmission Efficiency.	
Ans:	Define voltage regulation of transmission line:	(1 Marks)
	Voltage regulation is nothing but voltage drop in transmission	n line expressed
	in % of receiving end voltage	
	Sending End Voltage 🛮 Receiving End Voltage	
	% Regulation = Sending End Voltage Receiving End Voltage Receiving End Voltage	□100
	Treesining India vertage	
		1,
	$%regulation = \frac{No\ load\ receiving\ end\ voltage\ -\ Full\ load\ receiving\ end}{F.\ H.\ L.\ L.\ L.\ L.\ L.\ L.\ L.\ L.\ L.\ L$	$\frac{voltage}{100\%}$
	Full load receiving end voltage	
	Define Transmission efficiency:-	(1 Marks)
	TransmissionEfficency Output power at receiving end	
	Input power at sending end	
	☐ TOD Output(P _R)(Load(power)at reciving end)	□100
	☐ TOD Output(P _R)(Load(power)at reciving end) Output (PR)□Total losses	
	Where, PR is o/p power at receiving end	
	OR	
	% Efficiency =	
	PR □ 12RT □100 □ □ □ □ □ □ □ □ □ □ □ □ □ □ □ □ □	tance
	OR	
	% Efficiency =	
	$\frac{PR}{P_R \square 3 \square 2 R_{ph}} \square 100 \square \square$	ceof perphase
	OR	
	output power \$\pi_100	
	% Efficiency = $\frac{\text{output power}}{\text{output power}} \text{1100}$	

WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 6 of 27

Q. 2 Attempt any THREE of the following

12 Marks

a) Differentiate between overhead transmission and underground transmission.


Ans:

(Any Four points expected: 1 Mark each, Total 4 Marks)

S.No	Points	Overhead line	Underground cable
1	Capital cost	Less	More
2	Erecting cost	Less	More
3	Time require for completion of work	Less	More
4	Flexibility	More flexibility	No flexibility
5	Future expansion in voltage level	System voltage can be increased easily	System voltage cannot be increased
6	Overload capacity	More	Less
7	Fault finding	Easy	Difficult
8	Charging Current	Less	More
9	Chances of fault	More	Less
10	Chances of accident	More	No chances of accident
11	Safety	Less	More
12	Radio interference	Produces radio interferences	Not produces radio interferences
13	Short cute route	Difficult	Possible
14	Theft Of energy	More possibility	Less possibility
15	Voltage drop	More	Less
16	Power factor	Less	More
17	Reliability	Less	More
18	Life	Less	More
19	Space consumed	Space consumed	No space consumed
20	Appearance	Not good	Very good

WINTER-2019 Examinations

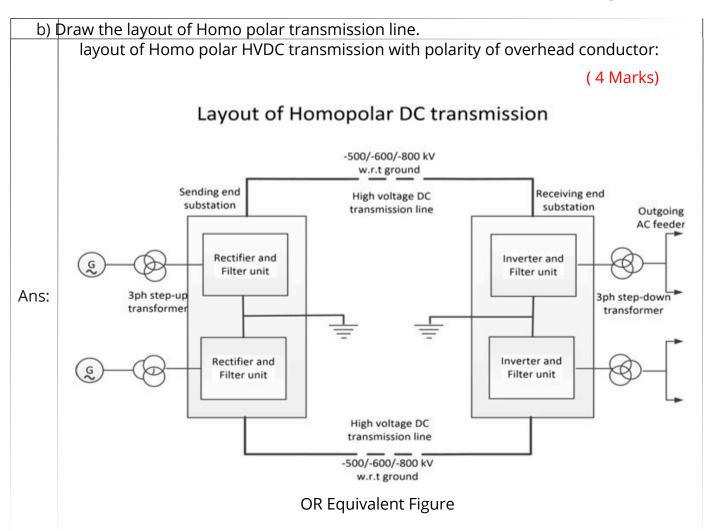Subject Code: 22419 <u>Model Answer</u> Page 7 of 27



c) \$tate the advantages of use of high voltage in transmission of Electric power.

Ans: | Advantages:

(Any Four points expected: 1 Mark each, Total 4 Marks)

- 1. As Transmission voltage increases, current decreases.
- 2. As current decreases, cross section of conductor decreases.
- 3. As cross section of conductor decreases, its weight decreases.
- 4. As weight of the conductor decreases, design of tower becomes lighter in weight.
- 5. As current decreases, cross section of bus bar and size of switch gear contact etc. reduces.
- 6. Due to above advantages, Transmission cost per KM decreases
- 7. As transmission voltage increases. A current decreases, so copper losses in transmission line reduces.
- 8. As copper losses reduces, transmission efficiency increases
- 9. As current reduces, voltage drop in transmission line reduces.
- 10. As voltage drop in transmission reduces, voltage regulation becomes better

WINTER-2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 8 of 27

(improved).


- 11. As efficiency and regulation of transmission line gets improved, so performance of transmission line increases
- 12. As transmission voltage increases power handling capacity of transmission line increases
- 13. Due to high voltage transmission line, successful interconnection of transmission line is possible than low voltage.
- d) Draw the layout of power system indicating Generation, Transmission and distribution parts.

 Single line diagram of AC electric transmission and distribution system:

Layout of Electric supply System

(4 Mark)

OR

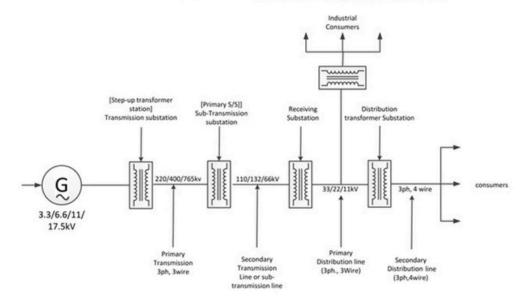

Block diagram of Power System

Generation → Step-up Substaion → Transmission → Step-down Substation → Distribution → (Consumer)

OR

or equivalent figure

WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 9 of 27

Q.3 Attempt any THREE of the following


12 Marks

a) Draw the diagram representing transposition of conductor and state its importance.

Ans: (Figure : 2 Mark Importance of Transposition: 2 Mark, Total 4 Marks)

Figure of transposition of conductor:

(2 Marks)

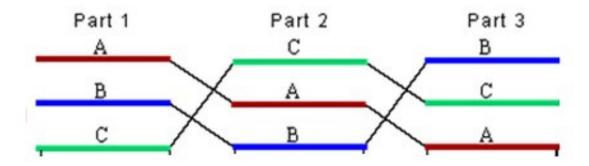

OR Equivalent Figure

Transposition of conductor means exchanging the position of 3 phases (R-Y-B) at regular interval.

Each phase occupies 3 different positions consequently on line support (Tower) as shown in fig.

OR

Transposition of line conductors means changing the positions of 3 phases on the line supports twice over the total length of the line

The Importance of transposition of conductors:

(2 Marks)

Due to transposition of conductor voltage at receiving end between any two phases are same

b) \$tate the standard voltage in India for Generation, transmission distribution system.

Ans: Standard voltage in India for Generation, transmission distribution system: (4 Marks)

1. Generation Voltage:

3.3KV, 6.6KV,11KV and 17.5 KV

2. Transmission voltage :- (Any four voltage magnitude are expected) 400KV, 765 KV (750 KV) ,220 KV, 132 KV, 110 KV, 33 KV, 22KV, 11 KV for

long distance line it may be 66 KV

OR

		WINTER- 2019 Examinations	
Su	bject Co	ode: 22419 Model Answer	Page 10 of 27
		☐ Primary Transmission voltage :-	
		□220 KV, 400KV, 765 KV (750 KV)	
		☐ Secondary Transmission:	
		□220 KV, 132 KV, 110 KV	
		☐ Primary Distribution:	
		33 KV, 22KV, 11 KV for long distance line it may be 66 KV	
	3. D	Distribution voltage :-	
		OR Secondary Distribution:	
		for3-phase, 400/440 Volt, for single phase 230 Volt	
c)		he factors to be considered while designing feeders and distrib · · · · · · ·	
Ans:	functi	ions in brief. (Factor of Feeder: 2 Marks & Distribution : 2 Marks, To	otal 2 Marks)
	Follov	wing factors are to be considered while designing the Feeder.	
		(Any Two factors are expected	: 1 Mark each)
	1)	Current carrying capacity of conductor:-	
		Conductor should have high current carrying capacity. While voltag	e drop
		consideration is relatively not so important	
		It is because voltage drop in feeder can be adjusted with the he	lp of tapings of
		distribution transformer manually or by using AVR (Automatic Voltage Reg	gulator)
	2)	Need:	
		Depending upon application design of distribution system should	be selected i.e.
		whether continuity of supply is important or not so important	
		Example: 1) Use Radial distribution system in rural area	
		2) Use Ring main distribution system in urban area	
		3) Use Grid distribution system where continuity of supply is important	t.
		e.g. Supply to - electric traction, TV broadcasting centre, AIR, telephor	ne exchange,
		major hospitals, important government buildings and major industries	
	3)	Availability of power: It should be available whenever needed	
	4)	Maintenance: It should be low, easy, less costly & less time consuming	<u>5</u> .

WINTER- 2019 Examinations

Subject Code: 22419 Page 11 of 27
Model Answer

5) Power Factor of load should be consider while designing

Following factors are to be considered while designing a distributor:- (Any Two factors are expected: 1 Mark each)

- 1. While designing the distributor voltage drop calculation is important.
- 2. Voltage drop in distribution system should be maintained within permissible limit (

 6%).
- 3. Layout should be simple in design.
- 4. It should have less initial cost
- 5. Make the distribution system with minimum distribution losses.
- 6. From safety point of view distribution system should maintain proper clearances.
- 7. Select the cross section of conductor from the result of load densities present & future.
- 8. While selecting cross section of conductor P.F. of the load should be consider.
- 9. Power should be available to consumers whenever needed.
- 10. A steady, non-fluctuating, quality supply (Pure sine wave) should be available to consumers.
- 11. Distribution system should not be over loaded.
- 12. Distribution system lay out should not affect the appearance of locality.
- 13. Before installation of distribution system proposed widening of the road in the near future are to be kept in mind
- 14. Fault on nearest distribution system should not affect stability of existing distribution system.

WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 12 of 27

d): Ans:	State advantages and disadvantages of radial distributor system. (Advantages : 2 Marks & disadvantages: 2 Marks, Total : 4 Marks)
Α113.	Advantages of radial distributor system: (Any Two point expected)
	1. Design of layout is simple.
	1. Design of tayout is simple.
	2. Capital cost & Erecting cost is less as there is only one feeder.
	3. Time required for completion of work is less.
	Disadvantagesof radial distributor system: (Any Two point expected)
	1. No reliability to maintain supply to consumers when there is fault on feeder.
	2. No reliability to maintain supply to consumers when there is maintenance on feeder.
	3. Voltage fluctuations are more.
Q.4	Attempt any THREE of the following 12 Marks
a)	list classification of distributor system with their advantages each. (any two)
Ans:	(4 Marks) According to scheme of connection there are three types of distribution systems: -
	1. Radial (Tree) distribution system
	•
	2. Ring mains (Loop) distribution system
	3. Grid (interconnected) distribution system
	1. Advantages of Radial (Tree) connection scheme:- (1 Marks)
	1. Design of layout is simple.
	2. Capital cost & Erecting cost is less as there is only one feeder.
	3. Time required for completion of work is less.
	2. Advantages of Ring Main System of distribution: (1 Marks)
	1 Supply to distribution transformer center is given through two different Feeders
	. Reliability to maintain supply is more even when there is a fault on any one feeder.
	2 Reliability to maintain supply is more even when there was maintenance on any one
	. feeder.
	3

WINTER- 2019 Examinations

Su	bject Code: 22419 Model Answer	Page 13 of 27
	3. Advantages of Grid or interconnected system of distribution:-	(2 Marks)
	Supply to distribution transformer center is given through two different g stations or major generating stations	generating
	It has highest reliability to maintain supply even when there is a fault on feeder	any one
	3. It has highest reliability to maintain supply even when there was mainten one feeder.	nance on any
	A 3-ph overhead line supported by 6 disc insulators, the potential of the following shunt capacitance between each insulator and each 1/5th of capacitance of insulator. Calculate: (i) line voltage (ii) string efforts and the following string of the following string string of the following string string of the following string	h metal link is o
Ans:	V6 = 11 KV	
	i) Ratio of capacitance 'm' :-	
	$m=\frac{1}{5}\square 0.2$	
	k = m = 0.2	(1/2 Mark)
	ii) V = 6 V1 (1 + 15m+ 35m ² +28m+ ⁹ m +m ⁴) ⁵	
	V ₆ □V 1(1 □15 □0.2 □35 □(0.2) 2□ 28 □(0.2) 3□9(0.24□) (02)5)	
	11D 5.638 V1	
	$V1 = \frac{11}{5.638}$	
	V1 = 1.951 KV	
		(1/2 Mark)
	iii) $V = V_5(1 + 1_0m + 15m2 + 7m3 + 9m4 + m5$	
	V ₆ []1.951(1[]10[]0.2[]15[](0.2)2[]7[](0.2)3[] ()]24	
	V5□1.951 (3.365)	
	V5 = 7.135 KV	·{ 1/2 Mark)
	iv) $V = {}_{4}$ $V1 1 + 6m + 5m^{2} + m)^{3}$	(1/2 Mark)

WINTER- 2019 Examinations

Subject Code: 22419 **Model Answer** Page 14 of 27 $V4 \square 1.951 (1 \square 6 \square 0.2 \square 5 \square (0.2) 2 \square (0.2) 3)$ V4 [] 1.951 (2.408) V4 = 4.69 KV -----(1/2 Mark) $V) V = V (1 + 3m + m^2)$ V3[]V1(1[]3[]0.2[](0.2)2) □ 1.951(1.64) V3 = 3.2 KV -----(1/2 Mark) vi) V20V1(10m) V201.951(100.2) $V2 = 1.951 \times 1.2$ V2 = 2.3412 vii) Voltage across string = Vph = V1 +V2+ V3+V4+V5+V6 = 1.95 + 2.3412 + 3.2 + 4.69 + 7.13 + 11VPh= 30.3112 KV -----(1/2 Mark) viii) The line voltage: $V_{\overline{t}} = \sqrt{3}Vph$ $VL = \sqrt{3} \, \Box 30.3112$ VL = 52.50 KV ----- (1/2 Mark) ix) String efficiency:-

WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 15 of 27

String % \square $\frac{\text{votage across whole string (Vph }\square \text{ V/}\sqrt{3}\text{ })}{\text{n }\square\text{ voltage across disc nearer to conductor}}\square100$

String
$$\square \% \square \frac{Vph}{n\square Vn} \square 100$$


String
$$\square \% \square \frac{30.3112}{6011} \square 100$$

String 00045.92600/

-----(1/2 Mark)

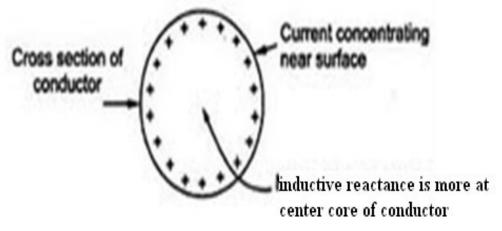c) \$tate the meaning of skin effect and how can it be minimised.

Ans: (Meaning : 2 Marks and effect minimized : 2 Marks, Total 4 Marks)
Meaning of skin effect



OR equivalent figure

When alternating current flows through conductor it has tendency to flow away from center of conductor.

i.e. maximum current density is near skin of conductor and goes on reducing towards centre core is known as skin effect. (Since the inductive reactance (XL) at the centre of the conductor is more than surface of conductor)

OR

The tendency of alternating current to concentrate near the surface of a conductor is known as skin effect.

WINTER-2019 Examinations

Subject Code: 22419 Page 16 of 27


Model Answer

Skin effect can be minimized by: (Any two points are expected)

- 1. Use stranded conductors instead of solid conductors.
- 2. Use hollow conductors instead of solid conductor.
- 3. Use ACSR /AAAC conductors for transmission purpose
- 4. Use D.C. supply whenever possible as Skin effect is absent (Since frequency 0) instead of A.C. supply.
- d) Draw the diagram of pin type and suspension type insulators.


Ans: | i) Neat labelled diagram of Pin type Insulator :

(2 Marks)

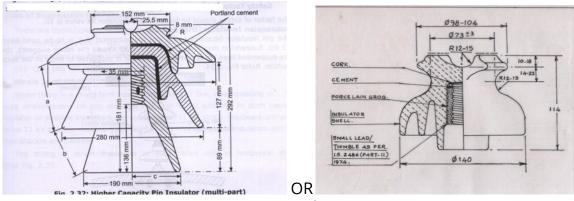

OR Equivalent Figure

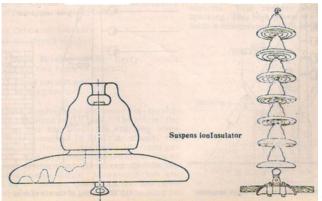ii) Neat labelled diagram of Suspension type Insulator : (2 Marks)



OR Equivalent Figure

e) State the effects of low power factor on efficiency and voltage regulation of short transmission lines.

Ans:

WINTER-2019 Examinations

Subject Code: 22419 Page 17 of 27

Model Answer

i) Effect of Low power factor on efficiency:-

(2 Marks)

When power factor of load reduces current drawn by transmission line increases so copper losses in transmission line increases, hence transmission efficiency reduces.

ii) Effect of Low power factor on voltage Regulation:-

(2 Marks)

When power factor of load reduces current through transmission line increases, so voltage drop in transmission line increases so regulation increases. (Become Poor)

f) State the condition for selecting site for distribution substation.

Ans: | Following condition should be considered while selecting site for distribution sub-station:-

1. Near load center: (Any four points expected: 1 Mark each, Total 4 Marks)

Sub-station should be located near load center to reduce cost of Transmission and distribution lines and to reduce losses in it.

2. Easy access for transmission Line:

There should be easy access for incoming and outgoing line.

3. Easy access towards sub-station:-

There should be easy access towards sub-station for transportation of equipments and manpower etc.

4. Space(Land) available:

The land proposed for a substation should be normally level and open from all sides &sufficient land should be available for installation of sub-station and future expansion.

5. Atmospheric conditions:

Atmospheric condition in the area of sub-station should be clean and dry also There should be less atmospheric pollution.

6. Cost of land:

Cost of land should be less to reduce capital cost of sub-station.

7. Municipal restriction:

Where municipal restriction will not take any objection for required type building of

WINTER-2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 18 of 27

sub-station.

8. Staff amenities:

The site should be such that essential amenities must be available to staff like residential quarters, drinking water, school, hospital, public transportation, communication.

9. Bearing capacity of land (Hard land):

To reduce construction cost of building and for better foundation of equipment's land should have high bearing capacity.

10. Area free from earthquake:


To avoid damage to sub-station area should be free earth quake.

Q.5 Attempt any TWO of the following

12 Marks

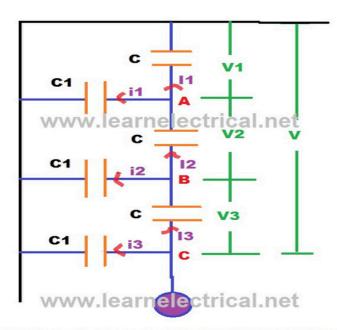a) Derive equation for string efficiency with 3 - disc insulators of suspension type.

Ans: Derive equation of String of three Disc insulators of suspension type:- (6 Marks)



Mathematical expression for String Efficiency

Mathematical proof:

Where,

WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 19 of 27

m \square $K \xrightarrow{C} \square$ 1 $C_1 \square$ mc
Step- I: Applying KCL to node 'A'
I20I10i1
V2UCUV1UCUV1UC1 But,C1Umc
V2[]C[]V1[]C[]V1[]mc
□V2□V1□V1m
0 V 2 0V1 (10 m) 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0 0
Step- II: Applying KCL to node 'B'
I30I20i2
V3 \square C \square V2 \square C \square (V1 \square V2) \square C ₁ But,C1 \square mc & V ₂ \square (m \square 1) V ₁ \square
$V3 \square C \square V1 (1 \square m) \square C \square V1 \square \ mc \square V1 (1 \square \ m) \square \ C$
V3[]V1(1[]m)[]V1m[]V1(1[] m)m
$V_3 \square V_1 (1 \square m \square m \square m \square m2)$
V ₃ 🗆 V ₁ (1 🗆 3 m 🗓 m 2) 🗆 🗆 🗆 🗆 🗆 🗆 🗆 🗆 🗆 🗆 🗆 🗆 🗆
V= V1 + V2+ V3
String Efficiency:-
Unequal potential distribution along a string of suspension insulator is usually
expressed in terms of string efficiency.
votogo porose whole string (Vah II) / /a)
String % \square votage across whole string (Vph $\square V/\sqrt{3}$) \square 100 \square voltage across disc nearer to conductor

WINTER-2019 Examinations

Subject Code: 22419 Page 20 of 27
Model Answer

iouel r

OR

String
$$\square \% \square \frac{Vph}{n \square Vn} \square 100$$

Where, n = Number of Disc insulators, Vn = Voltage across disc nearer to conductor\

b) Define Corona, List its causes and state how it can be avoided. (two each)

Ans: (Definition: 2 Marks, Causes: 2 Marks and corona avoided: 2 Mark, Total 6 Marks)

Define Corona: (2 Marks)

When AC Voltage given across two conductors separated by distance 'd' as shown figure is increased greater than breakdown voltage of air i.e. 30KV/cm, then air around the conductor gets ionized and ionized air is conducting under this condition corona will takes place (form).

During corona following observations are noted:

- Luminous violet glow (typically a purple glow) occurs around the conductor.
- Hissing or cracking sound will produce.
- ☐ Ozone gas will produce. (smell the presence of ozone that was produced by the corona)

This phenomenon is known as "corona" effect.

The following causes:- (Any Two points are expected)

(2 Marks)

1. Magnitude of Voltage:

If voltage across two conductors is greater than 30 KV/cm, i.e. breakdown voltage of air than corona formation starts. Corona will not start if voltage is below 30 KV/cm

2 Distance between two conductor:

If spacing between two conductors is very large as compare to their diameter than there is no possibility of corona formation. Because value of voltage at which corona occurs increases.

WINTER-2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 21 of 27

3. Size of conductor:

If size (Cross section) of conductor is more, than magnitude of voltage required to occur the corona increases.

4 Condition of conductor & Hardware:

Rough and irregular surface of conductor and hardware will give more corona than solid, smooth body conductor & hardware.

5. Atmospheric Condition:

As corona takes place due to ionization of air so it depends on condition of air so for dry air formation of corona occurs late than in wet air (damp atmosphere condition/rainy season/thunderstorms/fog air becomes more conductivity)

- 6 Effect of supply Frequency: Corona loss varies directly as the supply frequency
- . Effect of density of air: Corona loss increases with the decrease in the density of air (The
- 7 corona loss of transmission line passing through hilly area is higher than that of a similar
- . line in plain due to reduced value of air density at high level /altitude)

Corona effect can be avoided for following way: (Any Two points are expected) (2 Marks)

- 1 By increasing distance between two conductor i.e. by using longer cross arm.
- . By using larger size(diameter) of conductor e.g./ using ACSR, bundled conductor
- 2 By using smooth body conductor and hardware.

c) State the meaning of ferranti effect and proximity effect.

Ans:

i) Ferranti effect:

(3 Marks)


When long distance transmission is lightly loaded or there is no load condition than it is observe that receiving end voltage (VR) is found to be greater than sending end voltage (VS). This phenomenon is known as Ferranti effect.

WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 22 of 27

ii) Proximity effect:

(3 Marks)

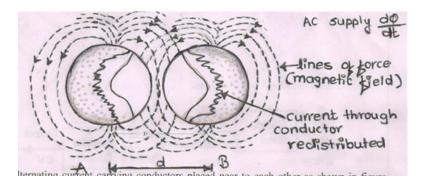

Explanation:

Let two alternating current carrying conductors placed near to each other as shown in figure. Due to electro-magnetic action, flux produced by each conductor links with each other. Due to this super –impose of magnetic field on conductor causes current in each conductor is re-distributed. This is known as proximity effect.

Q.6	Attempt any TWO of the following	12 Marks
	a) Compare nominal - T and nominal - II method of transm	ission line (Any six points)
Ans:		(Total: 6 Marks)


S.No.	Nominal T Method	Nominal 🗆 Method
1	It is assume that line capacitance is connected at centre of transmission line	It is assumed that capacitance of transmission line is divided into half of the line capacitance is connected receiving end & half of capacitance is connected at sending end.
2	It is assume that half of the resistance & reactance per phase are divided in either side of capacitance.	It is assumed that transmission line resistance & reactance per phase is connected between two half transmission line capacitance
3	Shape of equivalent circuit is like letter 'T' hence its name is nominal 'T' method	Shape of equivalent circuit is like letter 'l' hence its name is nominal 'l' method

MAHARASHTRA STATE BOARAD OF TECHNICAL EDUCATIOD (Autonomous)

(ISO/IEC-27001-2005 Certified)

WINTER- 2019 Examinations

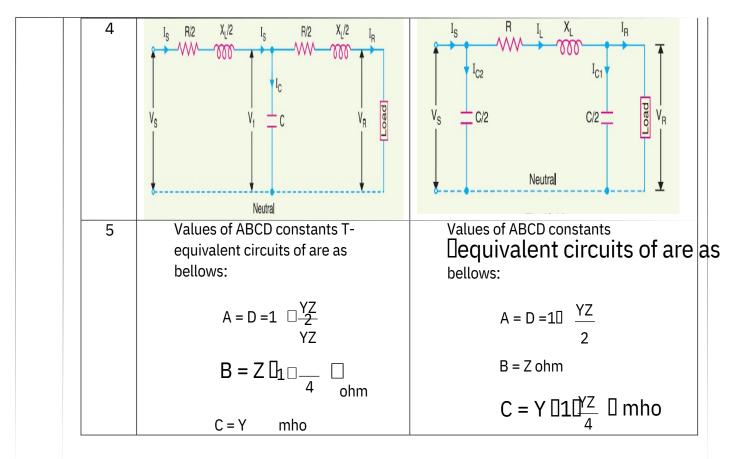Subject Code: 22419 **Model Answer** Page 23 of 27



b) \$tate the meaning of FACTS and explain in brief d-types facts controller.

Flexible AC Transmission System (FACTS):-Ans:

(3 Marks)

A flexible alternating current transmission system (FACTS) is defined as it is a system composed of static equipment used for the AC transmission of electrical energy. It is meant to enhance controllability and increase power transfer capability of the network. It is generally a power electronics-based system.

OR

A Flexible AC transmission System refers to the system consisting of power electronic devices along with power system devices to enhance the controllability and stability of the transmission system and increase the power transfer capabilities.

D-types facts controller:

(3 Marks)

Series Controllers: Series Controllers consists of capacitors or reactors which introduce voltage in series with the line. They are basically variable impedance devices. Their major task is to reduce the inductivity of the transmission line. They supply or consume

WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 24 of 27

variable reactive power. Examples of series controllers are SSSC, TCSC, TSSC etc. Shunt Controllers: Shunt controllers consist of variable impedance devices like capacitors or reactors which introduce current in series with the line. Their major task is to reduce the capacitivity of the transmission line. The injected current is in phase with the line voltage. Examples of shunt controllers are STATCOM, TSR, TSC, SVC. Shunt-Series Controllers: These controllers introduce current in series using the series controllers and voltage in shunt using the shunt controllers. Example is UPFC. Series-Series Controllers: These controllers consist of a combination of series controllers with each controller providing series compensation and also the transfer real power along the line. Example is IPFC.

OR

1. Shunt compensation

In shunt compensation, power system is connected in shunt (parallel) with the FACTS. It works as a controllable current source. Shunt compensation is of two types:

2. Shunt capacitive compensation

This method is used to improve the power factor. Whenever an inductive load is connected to the transmission line, power factor lags because of lagging load current. To compensate, a shunt capacitor is connected which draws current leading the source voltage. The net result is improvement in power factor.

3. Shunt inductive compensation

This method is used either when charging the transmission line, or, when there is very low load at the receiving end. Due to very low, or no load – very low current flows through the transmission line. Shunt capacitance in the transmission line causes voltage amplification (Ferranti effect). The receiving end voltage may become double the sending end voltage (generally in case of very long transmission lines). To compensate, shunt inductors are connected across the transmission line. The power transfer capability is thereby increased depending upon the power equation

4. Series compensation

FACTS for series compensation modify line impedance: X is decreased so as to increase the transmittable active power. However, more reactive power must be provided.

WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 25 of 27

(i) List the properties of line insulators in brief.

(ii) List the methods of Line Support Erection and explain in brief any one.

Ans:

Following are the properties of line insulators: (Any three properties are expected)

(3 Marks)

A) Electrical Properties of insulating material:-

It should have high resistance.

It should have high breakdown voltage.

It should have high dielectric strength.

It should have low dielectric loss.

It should have low dielectric constant.

- B) Mechanical Properties of insulating material:-
 - 4) It should have high mechanical strength.
 - 2) It should be tough and flexible.
 - 3) It should be light in weight.
 - 4) It should not be porous otherwise it increases moisture holding capacity which reduces insulating property.
- C) Chemical Properties of insulating material:-
 - 1 It should not be hygroscopic (which absorbs moisture).
 - . It should have high resistance to acid & alkaline (Chemicals).
 - 2 It should have high resistance to oil.
- D) Thermal Properties of insulating material:-

3

- 1 It should have high thermal conductivity.
- . It should be non-inflammable.
- 2 It should withstand at high temperature.
- . It should have thermal Stability.
- 3 Co-efficient of thermal expansion should be low.
- E) General Properties of insulating material:-


4

- 1 It should have longer life.
- 5 It should have low cost

2

WINTER- 2019 Examinations

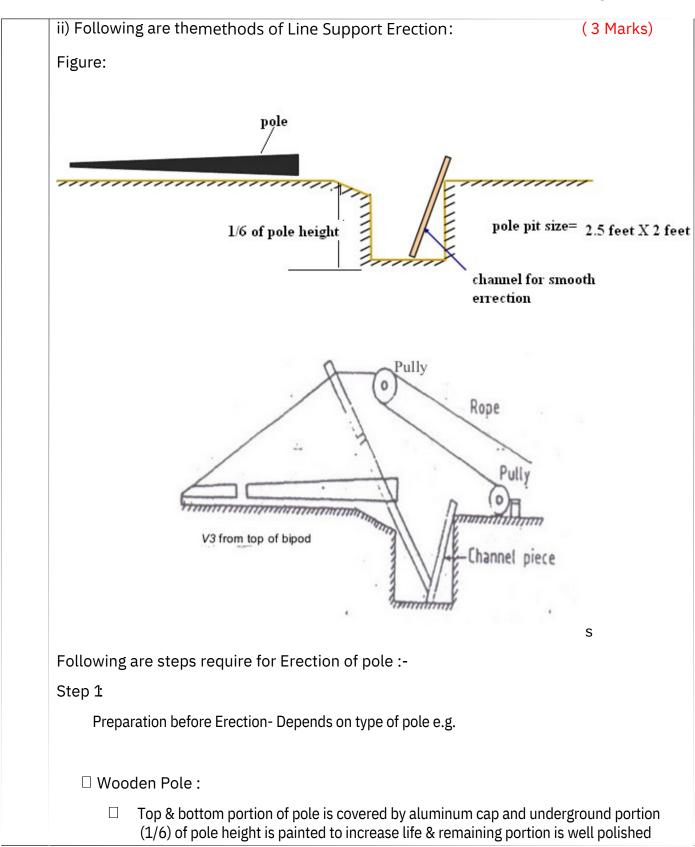Subject Code: 22419 <u>Model Answer</u> Page 26 of 27



WINTER- 2019 Examinations

Subject Code: 22419 <u>Model Answer</u> Page 27 of 27

	with the help of varnish.
	Cement Pole :
	$\hfill\Box$ 1/6 portion of pole height is No preparation is required like wooden pole and steel pole
	Steel Pole :
	□1/6 portion of pole height of steel pole which goes under ground is painted with bituminous paint to protect pole from rusting. Also base plate of mild steel is welder at bottom for better foundation.
	Steel towers:
	Are erected on site by constructing strong foundation (cement concrete foundation)
Step	2:
	Prepare a pit on given marking.
Step	3:
	Size of pit should be 2.5 feet X 2 feet and depth of pit 1/6 of the pole height.
Step	4:
R	lest the pole on channel for smooth and gradual Erection.
Step	5:
S	Erect a pole in a prepared pit using accessories (such as rope, pole, tripod etc.) and ufficient man power. Now a days machineries are used for Erection of pole.
Step	6:
Д	fter Erection of pole, check the alignment before concreting.
Step	7:
	low pour the concreting of ratio 1:4:8 in pole pit.

-----END------